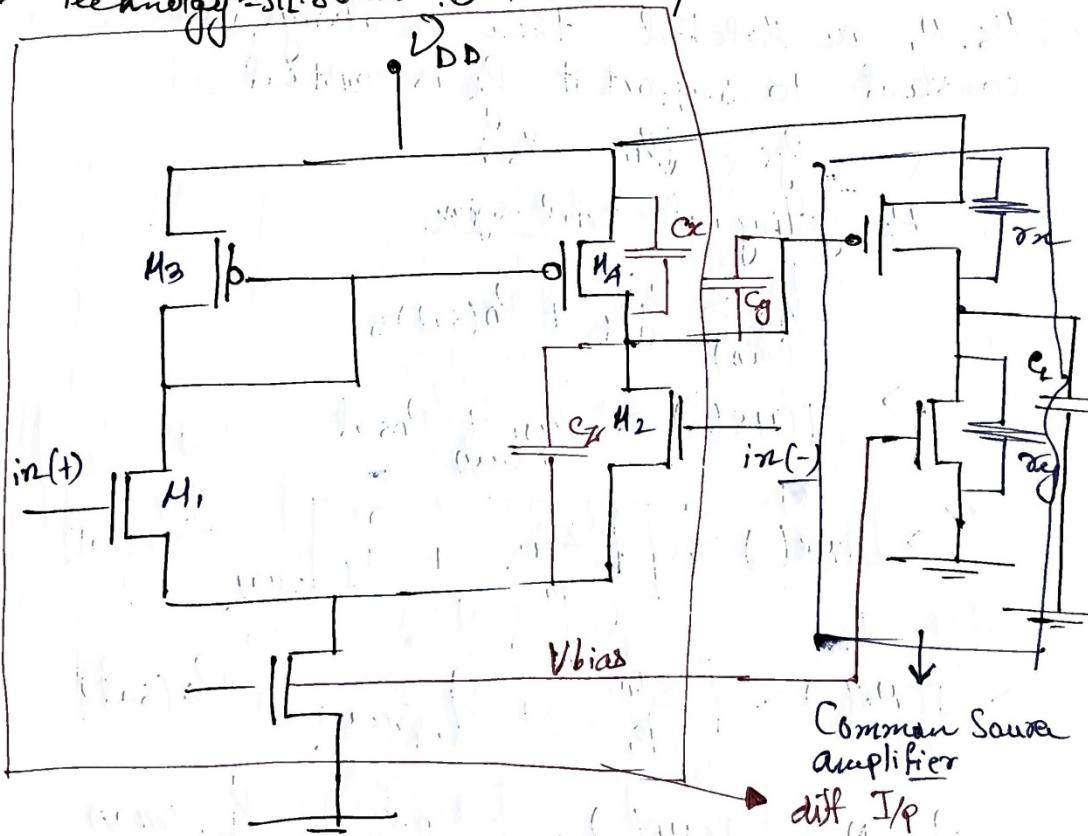


Design specifications


- ① DC gain = 60dB
- ② Phase Margin = 60°
- ③ slew rate = $20\text{V}/\mu\text{sec}$.
- ④ Power supply = 1.8V
- ⑤ Input common Mode ratio (+) = 1.6V
- ⑥ Input common Mode ratio (-) = 0.8V
- ⑦ Length = 180nm ~~GBW = 30MHz~~
- ⑧ Technology = SCL 180nm ~~power = $300\mu\text{W}$~~




$$\begin{aligned} \gamma_{dg} &= \gamma_x \parallel \gamma_y \\ C_1 &= C_2 \parallel C_y \parallel C_z \end{aligned}$$

$$C_L = C_2$$

Current Mirror
load

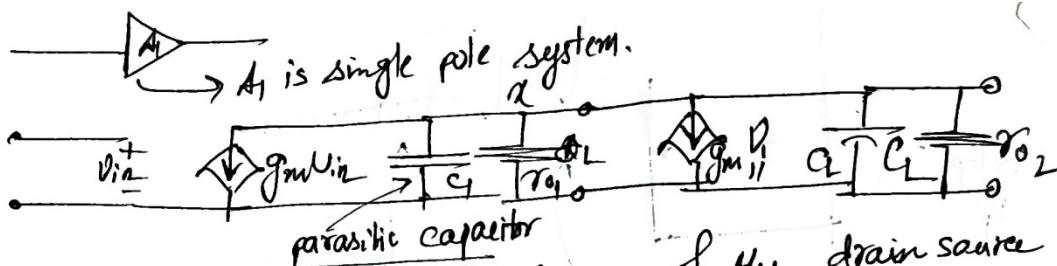

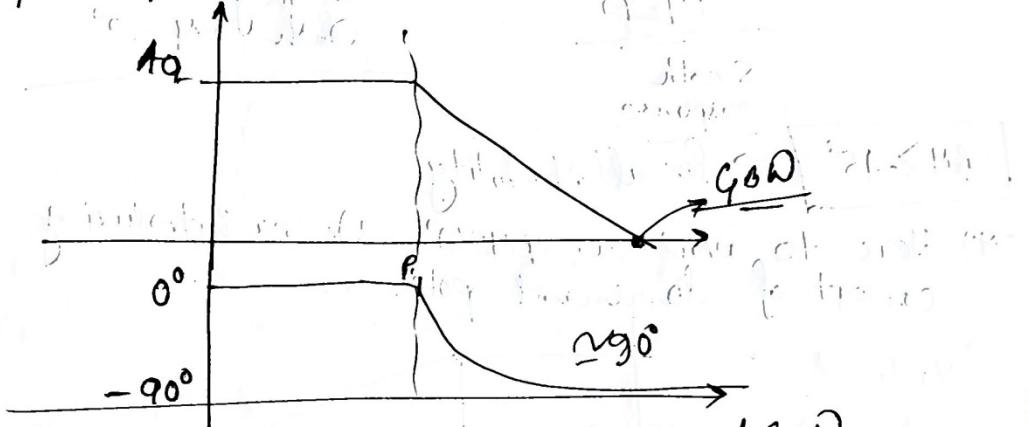
* This parasitic capacitor is gate cap. of M_2 , drain source capacitor of M_1 , drain source capacitor of M_2 .




Near -90° PM is considered as a soft PM. at GOW
Which is advantage

$$r_{02} \rightarrow r_{02} || r_{xy}$$

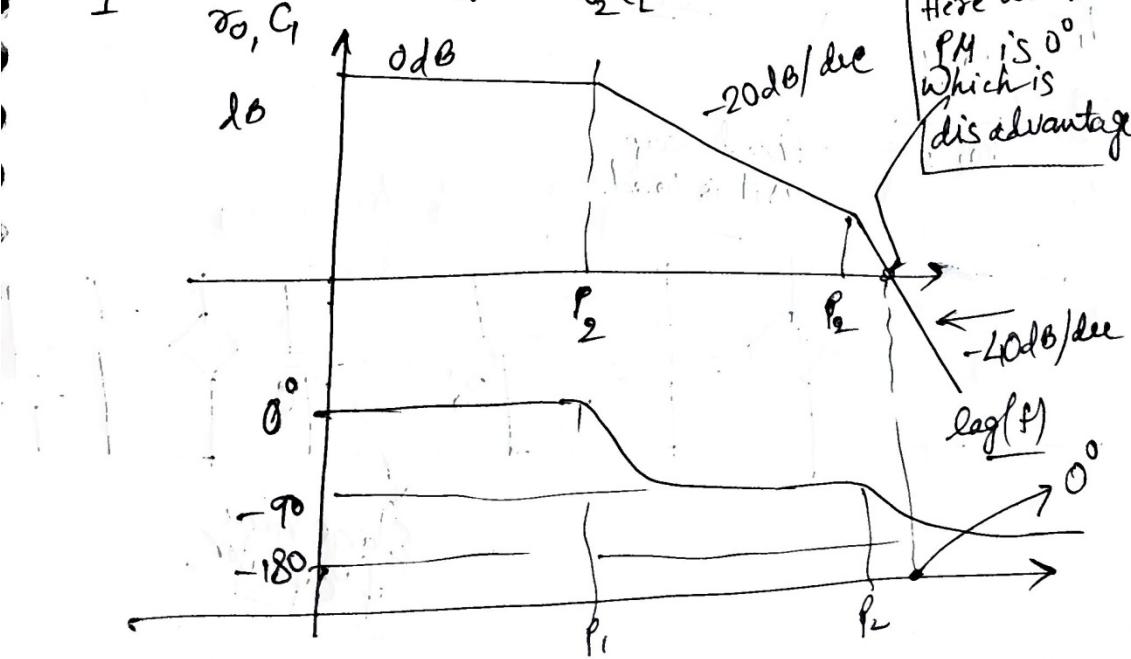
$$\rho_1 = \frac{1}{r_{01} C_1} \quad \rho_2 = \frac{1}{r_{02} C_2}$$



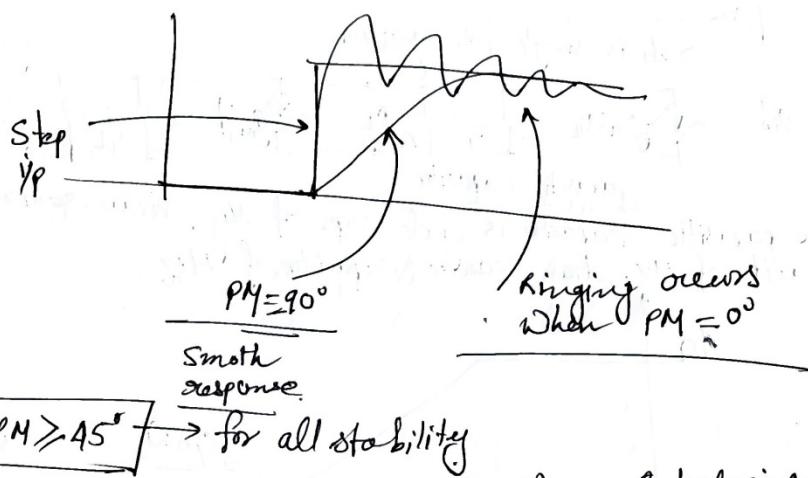

To avoid the Miller effect

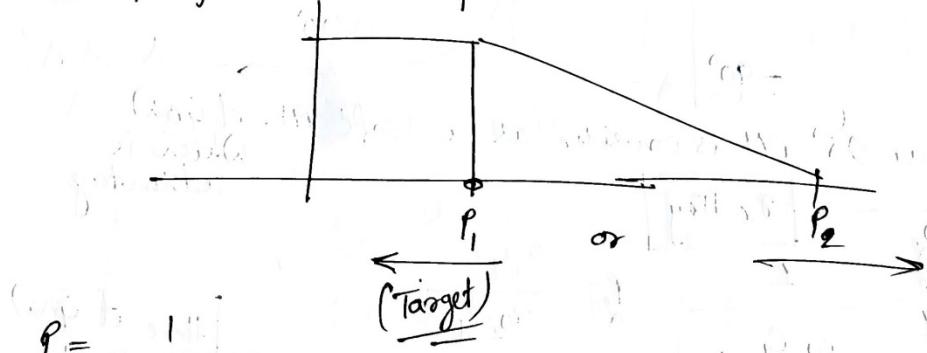
(*) Here to avoid the $PM = 0^\circ$. We are introducing concept of dominant pole.





Smooth s

+
V_{in}

—
Terms
= P₁
—
R₁
—
C₁

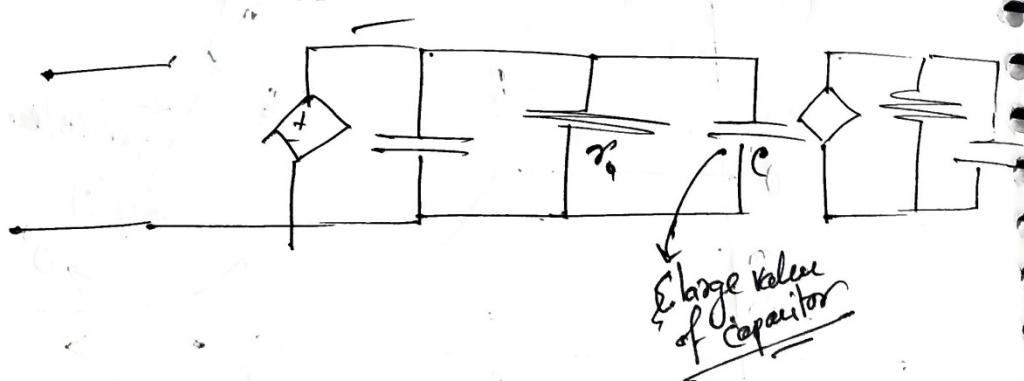

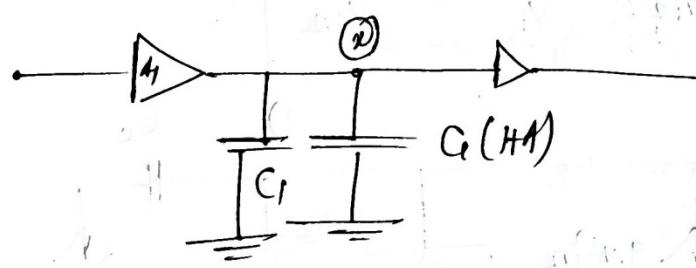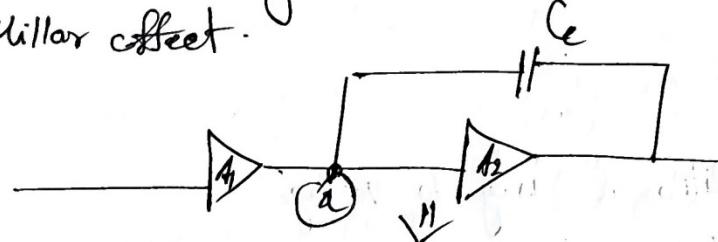
To avoid that big capacitance we introduce Miller effect.



$$\frac{V_o}{V_i} = \frac{1}{\tau_{01} (C_1 + C_c (1 + A))}$$

compensation capacitor


Small signal Model

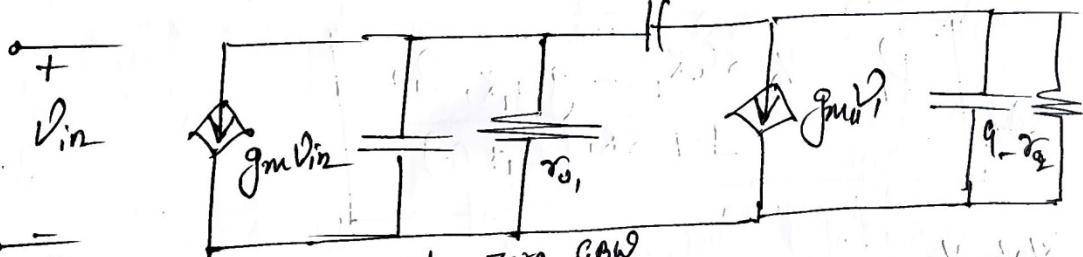

Terms
phase Margin - pole, zeros, GBW

- slew rate

- swings, limit

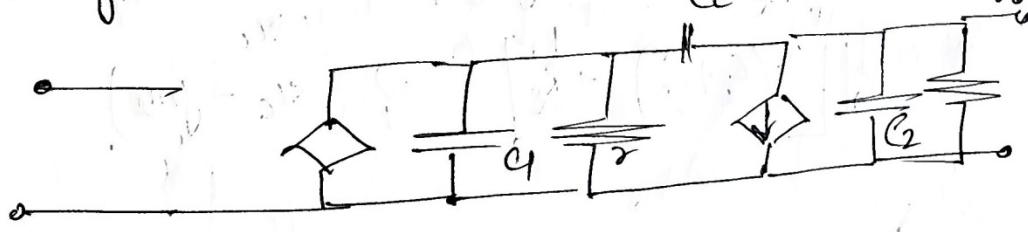


Miller Theorem has two disadvantages

- ① pole splitting
- ② zeros

So, To find traditional way to voltage
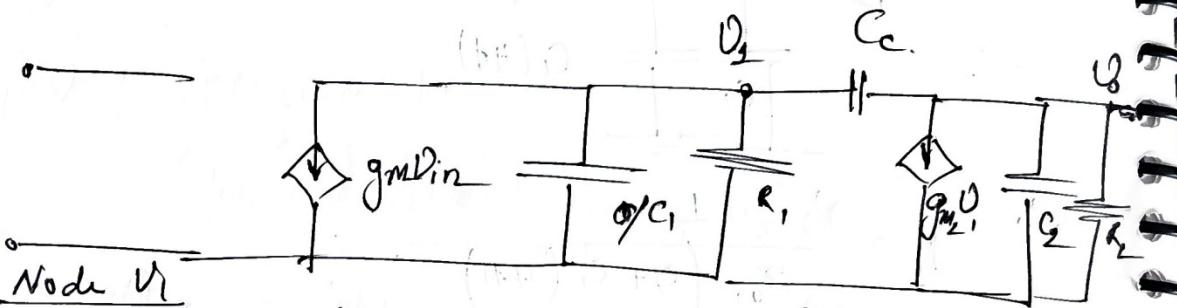
$$\frac{V_1}{V_{in}} \times \frac{V_o}{V_1} = \frac{V_o}{V_{in}}$$



Node V_1

$$\frac{V_1}{1/sC_1} + \frac{V_1}{R_1} + g_m V_{in} + \frac{V_1 - V_2}{1/sC} = 0$$

$$V_1 = \frac{V_2 s C_C R_1 - g_{m1} k_1 D_{in}}{1 + s R_1 (C_1 + C_C)}$$

Node V_2

$$\frac{V_2}{1/sC_2} + \frac{V_2}{R_2} + g_{m2} D_1 + \frac{V_2 - V_1}{1/sC} = 0$$

$$V_2 \left[\frac{s(C_2 + C_C)}{1/sC} + \frac{1}{R_2} \right] = D_1 (s C_C - g_{m2}).$$


$$V_o \left[s(C_2 + C_c) + \frac{1}{R_2} \right] = \frac{(V_o sC_c R_1 - g_m K_1 V_{in}) (sC_c - g_m)}{1 + s(C_1 + C_c) R_1}$$

$$\frac{V_o}{V_{in}} = \frac{g_m K_1 g_m R_2 \left(1 - \frac{sC_c}{g_m^2} \right)}{s^2 \left[R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c) + s(R_2(C_1 + C_c) + R(C_c + C_1) + C_c g_m R_2 K_1 R_2) \right]}$$

As we know for any std 2 pole system + 1 and one zero is

$$\frac{V_o}{V_{in}} = \frac{A_{oe} \left(1 - \frac{s}{P_2} \right)}{\left(1 + \frac{s}{P_1} \right) \left(1 + \frac{s}{P_2} \right)}$$

$A_{oe} \rightarrow$ DC gain of opamp

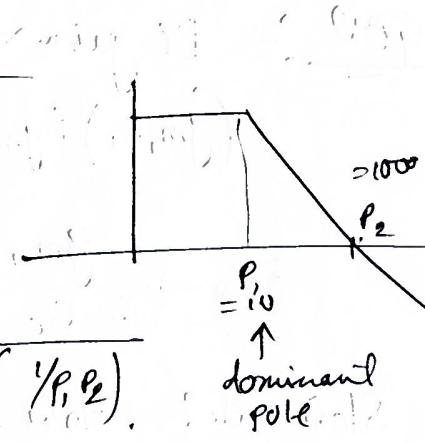

$$= \frac{A_{oe} \left(1 - \frac{s}{P_2} \right)}{1 + s \left(\frac{1}{P_1} + \frac{1}{P_2} \right) + s^2 \left(\frac{1}{P_1 P_2} \right)}$$

so, $s \left(\frac{1}{P_1} + \frac{1}{P_2} \right) \approx s \left(\frac{1}{P_1} \right)$

$\frac{1}{P_1} \rightarrow$ Co-eff of s

$$\text{Co-eff } s^2 \Rightarrow -\frac{1}{P_1 P_2} / P_1 P_2$$

$$P_1 = \frac{1}{R_2(C_1 + C_c) + R(C_c + C_1) + C_c g_m R_2 K_1 R_2}$$

$$P_1 P_2 = \frac{1}{R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c)} \approx \frac{P_1 P_2}{C_c g_m R_1 R_2} \quad \text{large}$$

$$P_2 = \frac{1}{R_1 R_2 (C_1 C_2 + C_1 C_c + C_2 C_c)} \quad \begin{aligned} C_c &\rightarrow \text{parasitic cap} \\ C_c &\rightarrow \text{Comp. cap} \\ C_c &\rightarrow \text{load cap} \end{aligned}$$

$$= \frac{(C_1 C_2 + C_1 C_c + C_2 C_c)}{C_c g_m R_1 R_2} \approx \frac{C_c g_m R_1 R_2}{C_c C_2} \approx \boxed{\frac{g_m L / C_2}{C_c} = P_2}$$

Zero location

$$1 - \frac{sC_c}{g_m R_2} = 0$$

$$s = -\frac{g_m R_2}{C_c}$$

$$A_{op} = (s=0) = -g_m_1 g_m_2 R_1 R_2$$


G_{BW} :- DC gain $\times P_1$

$$= (g_m_1 R_1) (g_m_2 R_2) \times \frac{1}{g_m_2 R_1 g_m_2 C_c}$$

$$= \frac{g_m_1}{C_c}$$

Slew rate :- How much quickly o/p can change

w.r.t V_{in}

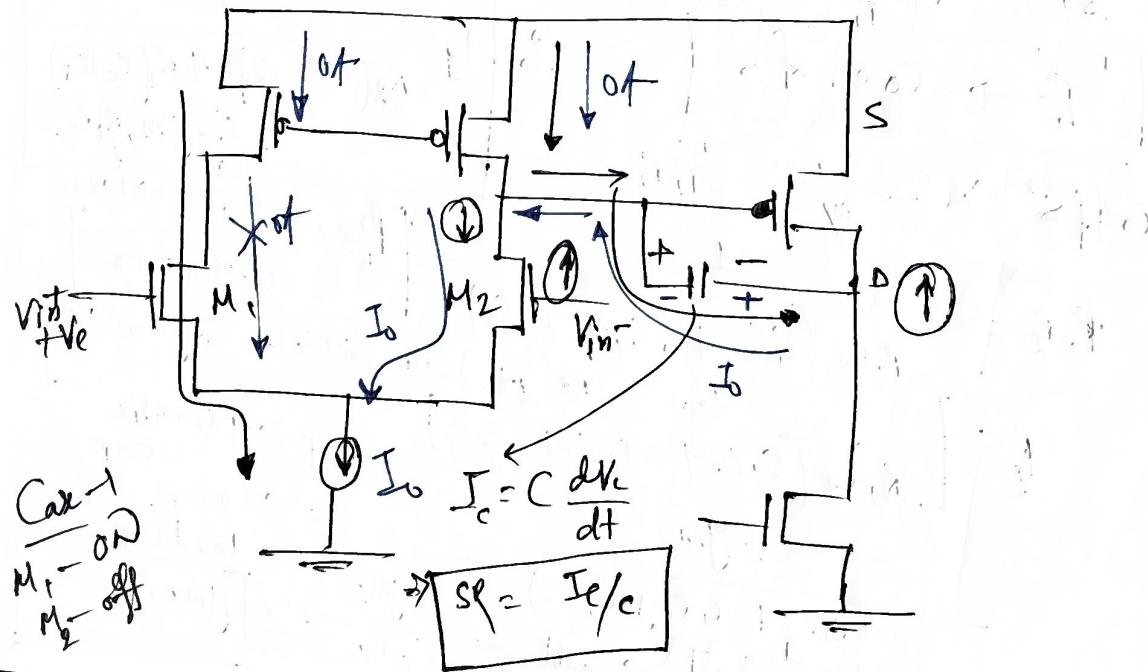



Case-II $H_2 \rightarrow ON$
 $H_1 \rightarrow off.$

Phase Margin:-

$$Z \geq 10GBW \quad (1)$$

Assume
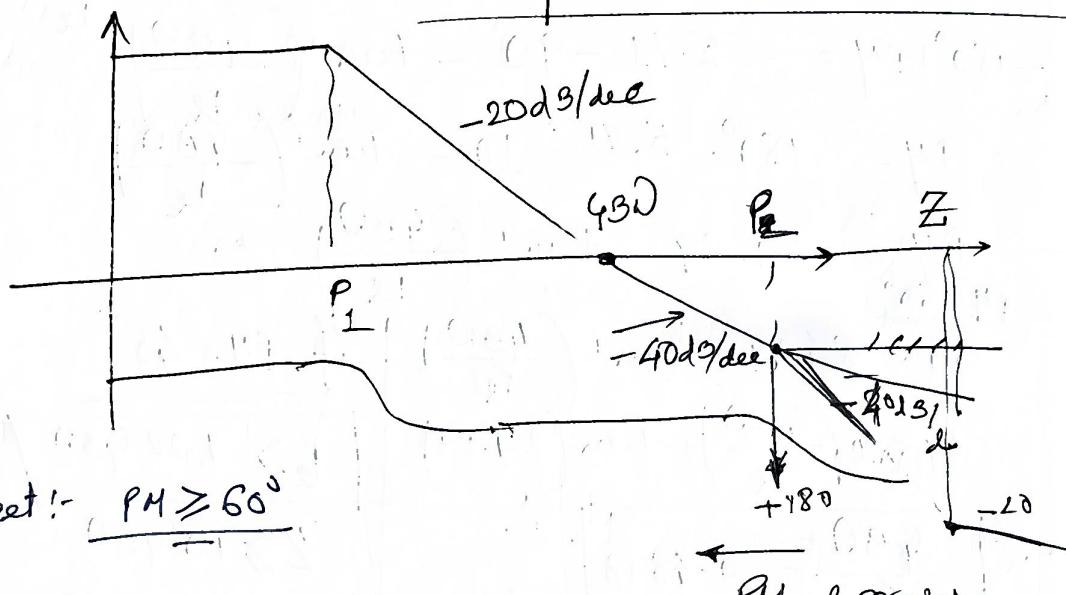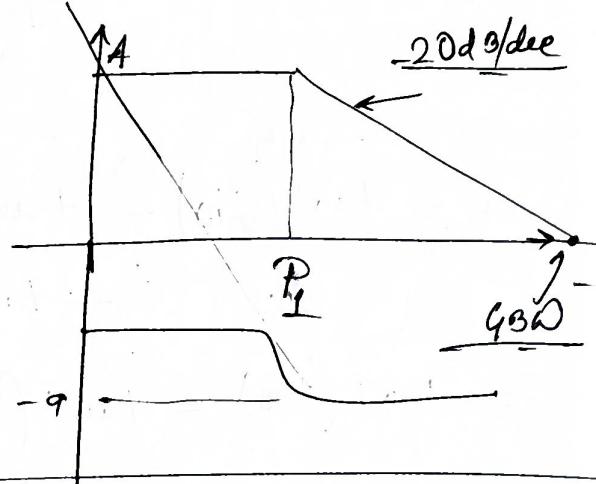
$$\frac{\angle V_o}{V_{in}} = -\tan^{-1}\left(\frac{\omega}{Z}\right) - \tan^{-1}\left(\frac{\omega}{P_1}\right) - \tan^{-1}\left(\frac{\omega}{P_2}\right) - \alpha$$



Target:- $PM \geq 60^\circ$

(*) $\frac{\angle V_o}{V_{in}} = -\tan^{-1}\left(\frac{\omega}{Z}\right) - \tan^{-1}\left(\frac{\omega}{P_1}\right) - \tan^{-1}\left(\frac{\omega}{P_2}\right)$

$$PM = +180^\circ + \angle G(j\omega)$$

$$Z \geq 10GBW$$

$$\angle G(j\omega) = -180^\circ + PM$$

$$\Rightarrow \frac{\angle V_o}{V_{in}} = -\tan^{-1}\left(\frac{\omega}{Z}\right) - \tan^{-1}\left(\frac{\omega}{P_1}\right) - \tan^{-1}\left(\frac{\omega}{P_2}\right) - \tan^{-1}\left(\frac{GBW}{\omega_f}\right) - \tan^{-1}\left(\frac{GBW}{P_1}\right) - \tan^{-1}\left(\frac{GBW}{P_2}\right)$$

$$\frac{V_o}{V_{in}} = -\tan^{-1}\left(\frac{G_B \omega}{10 g_m \omega}\right) - \tan^{-1}\left(\frac{g_m L_1 g_m L_2 C_L}{C_L}\right)$$

$$- \tan^{-1}\left(\frac{g_m L_1}{C_L g_m L_2}\right)$$

$$= -\tan^{-1}(1/10) - \tan^{-1}(g_m, g_m L_2 R_1 C_L)$$

$$- \tan^{-1}\left(\frac{g_m C_L}{C_L g_m L_2}\right)$$

$$= -\tan^{-1}(1/10) - \tan^{-1}(A_{DC}) - \tan^{-1}\left(\frac{G_B \omega}{P_2}\right)$$

$$-180^\circ + PM = -5.71 - 90^\circ - \tan^{-1}\left(\frac{G_B \omega}{P_2}\right)$$

$$PM = 180^\circ - 5.71 - 90^\circ - \tan^{-1}\left(\frac{G_B \omega}{P_2}\right)$$

$$PM = 84.29 - \tan^{-1}\left(\frac{G_B \omega}{P_2}\right)$$

$$\text{if } PM = 60^\circ$$

$$60 = 84.29 - \tan^{-1}\left(\frac{G_B \omega}{P_2}\right)$$

$$\tan\left(\frac{G_B \omega}{P_2}\right) = \tan(24.29)$$

$$\boxed{\frac{G_B \omega}{P_2} = 0.4513}$$

$$P_2 = \frac{G_B \omega}{0.4513}$$

$$\boxed{P_2 = 2.2 G_B \omega}$$

$$\frac{g_m L_2}{C_L} > (2.2) \frac{g_m L_1}{C_L}$$

$$\frac{10 g_m L_1}{C_L} > (2.2) \frac{g_m L_1}{C_L}$$

if $PM = 45^\circ$

$$\boxed{P_2 \geq 1.22 G_B \omega}$$

$$2 \geq 10 G_B \omega$$

$$\frac{g_m L_2}{C_L} \geq 10 \frac{g_m L_1}{C_L}$$

$$\boxed{g_m L_2 \geq 10 g_m L_1}$$

$$\boxed{\frac{10}{2} > 2.2 C_L}$$

∴

DC g

G B
P r
S t e

I n p u t
I C

P o
Des



$$\therefore C_L \geq 0.22 C_L$$

Design procedure

Design

$$DC\ gain = 1000 = 60dB$$

$$GBW = 30\text{Hz}$$

$$PM > 60^\circ$$

Slew rate = 20V/μsec

Input common mode ratio (ICMR) = 1.6

$$ICMR(-) = 0.8V$$

$$C_L = 2\text{pF}$$

$$Power \leq 300\mu\text{W}$$


Design of M₁, M₂

$V_{DD} = 1.8V$
process Tech = 180nm

1.6V

$L_{min} = 180\text{nm}$

$L = 500\text{nm}$
channel length

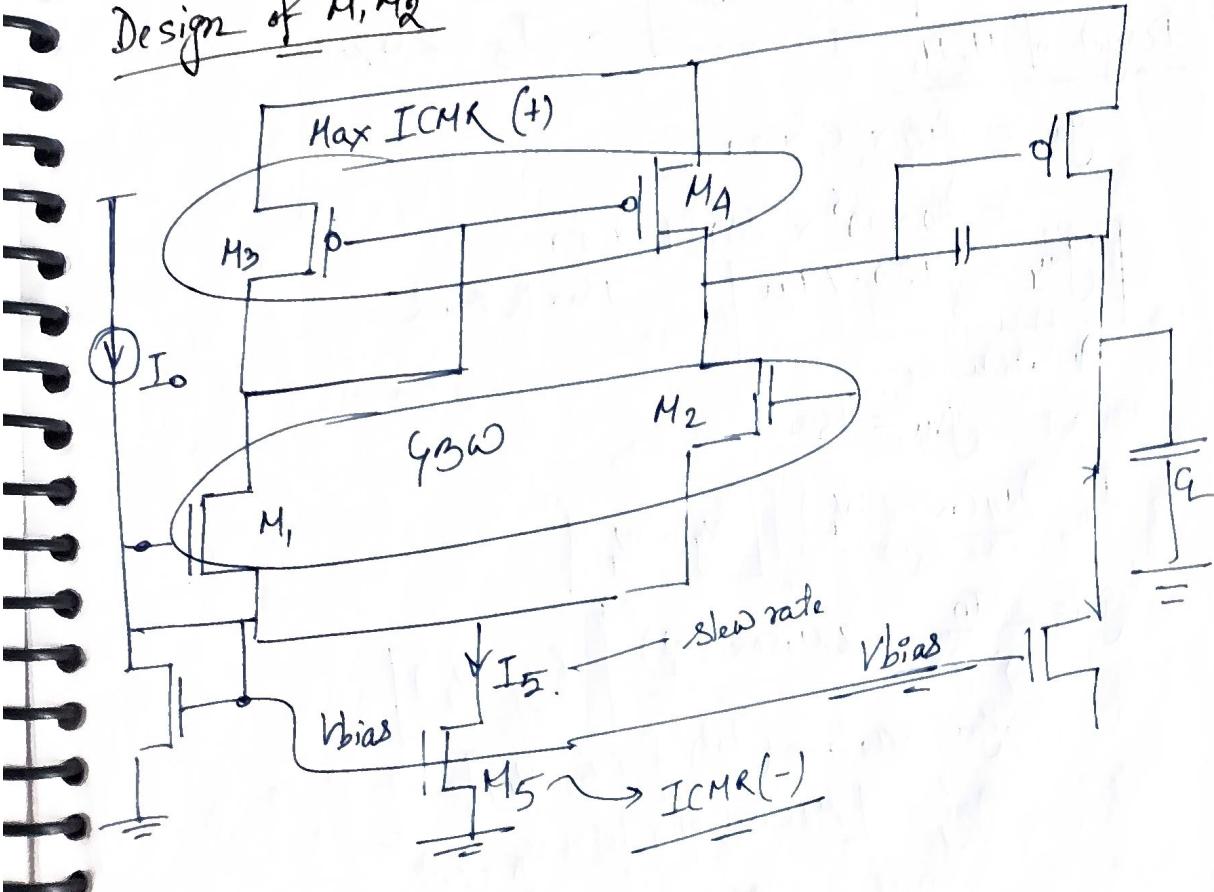

$$① L = 500\text{nm} \quad \text{Assume } C_L = 2\text{pF}$$

$$② C_C \geq 0.22 C_L$$

$$C_C \geq 0.22 \times 2\text{pF}$$

$$C_C \geq 0.44\text{pF}$$

$$\boxed{C_C \geq 440\text{fF}}$$

$$\boxed{C_C = 800\text{fF}}$$

$$③ S_C = 20\text{V}/\mu\text{sec.} = \frac{I_5}{C_C}$$

$$I_5 = \frac{20\text{V}}{\mu\text{sec}} \times 800\text{fF}$$

$$\boxed{I_5 = 16\mu\text{A}} \xrightarrow{\text{Min}} I_5 = 20\mu\text{A}$$

Design of M_1, M_2

$$g_{m1} = qB \times C_C \times 2\pi$$

$$= 30 \times 10^6 \times 800\text{fF} \times 2\pi$$

$$\boxed{g_{m1} = 150.79\mu} \xrightarrow{\text{This is Min}}$$

We assume,

$$\boxed{g_{m1} = 160}$$

$$I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) \left[V_{GS} - V_T \right]^2$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{2\mu_n C_{ox}}{2} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) \right]$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L} \right) \left[(V_{GS} - V_T) \right]$$

$$g_m^2 = \left[\mu_n C_{ox} \left(\frac{W}{L} \right) \right]^2 \left(V_{GS} - V_T \right)^2$$

$$= 2 I_D \left(\mu_n C_{ox} \left(\frac{W}{L} \right) \right)^2 \times 2$$

$$\left(\frac{W}{L}\right) = \frac{g_m^2}{\mu_n C_{ox} 2 I_D}$$

for M_1, M_2
 $\frac{2 I_D}{2 I_D} = I_S$


$$\left(\frac{W}{L}\right)_{1,2} = \frac{g_m^2}{\mu_n C_{ox} 2 I_D} I_S$$

$$= \frac{160^2}{300 \times 20} \approx 4.266$$

$$\boxed{\left(\frac{W}{L}\right)_{1,2} = 5}$$

Design of M_3, M_4

V_{DD}

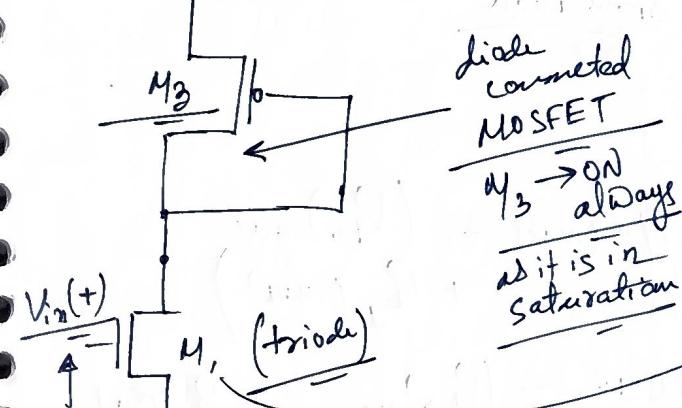


dissimilar connected
MOSFET
 $M_3 \rightarrow ON$ always
as it is in saturation

for saturation

$$V_{DS} \geq V_{GS} - V_{TH}$$

$$V_{DS} \leq V_{GS} - V_{TH}$$

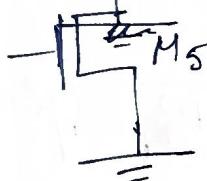M_1 enters to linear region as it is $V_{GS} \uparrow$



for M_1 to be in saturation

$$V_g < V_D + V_{TH}$$

$$V_{in} \leq V_D + V_{TH}$$

$$(V_{in})_{max} \leq V_D + V_{TH} \quad ①$$

$$D_1 = V_{DD} - V_{GS3}$$

$$I_{D3} = \frac{\mu_n C_{ox} (\frac{W}{L})}{2} (V_{GS} - V_{TH})^2$$

$$= \frac{\rho}{2} (V_{GS} - V_{TH})^2$$

$$V_{GS} = \sqrt{\frac{2 I_D}{\rho q}} + V_{TH}$$

$$\textcircled{1} \quad V_{D_1} = V_{DD} - \left[\sqrt{\frac{2I_{D_3}}{\rho}} + |V_{T3}| \right]$$

$$V_{in(\max)} \leq V_{D_1} + V_{T1}$$

$$\Rightarrow ICMR(+) \leq V_{D_1(\min)} + V_{T1(\min)}$$

$$V_{in(\max)} \leq V_{D_1(\min)} + (V_{T1})_{\min}$$

$$ICMR(+) \leq V_{DD} - \sqrt{\frac{2I_{D_3}}{\rho_3}} - |V_{T3}|_{\max} + V_{T1(\min)}$$

$$\boxed{\begin{array}{l} \mu_p C_{ox} = 60 \mu \\ \mu_n C_{ox} = 300 \mu \end{array} \quad \text{By simulation}}$$

$$\frac{2I_{D_3}}{\rho_3} = (V_{DD} - ICMR(\max) - (V_{T3})_{\max} + V_{T1(\min)})^2$$

$$\frac{2I_D}{\mu_p C_{ox} (N/L)_{3,4}} = V_{DD} - ICMR - (V_{T3})_{\max} + V_{T1(\min)}$$

$$(W/L)_{3,4} = \frac{2I_{D_3}}{\mu_p C_{ox} [V_{DD} - ICMR + V_{T3(\max)} + V_{T1(\min)}]^2}$$

$V_{T1} \rightarrow$ Threshold voltage of M_1

for Simulation,

$$V_{DD} = 1.8V$$

$$I_{D_3} = \frac{I_{DS}}{2} = 10 \mu A$$

$$\mu_p C_{ox} = 60 \mu$$

$$ICMR(+) = 1.6V$$

$$V_{T3}(+) = 0.50 \mu V$$

$$\therefore (W/L)_{3,4} = \frac{2 \times 10 \times 10^{-6}}{60 \times 10^6 [1.8 - 1.6 - 0.50 + 0.47]}^2$$

$$(W/L)_{3,4} = 13.02$$

$$\text{Assume } (W/L)_{3,4} = 14$$

$$B_{(sat)} \geq 0.8 - 0.115 \times 4 = 0.59$$

for Safety Margin $V_D(sat)_{\text{assume}} = (105 \text{ mV})^2$

$$\left(\frac{W}{L}\right)_S = \frac{2 \times 20 \times 10^{-6}}{30 \times 10^{-6} \times (105)^2}$$

$$\boxed{\left(\frac{W}{L}\right)_S \approx 12}$$


Design of M6

for 60°PM

$$\boxed{g_{m6} \geq 10 g_m}$$

$$g_{m6} \geq 10 \times (160 \mu)$$

$$\boxed{g_{m6} \geq 1600 \mu}$$

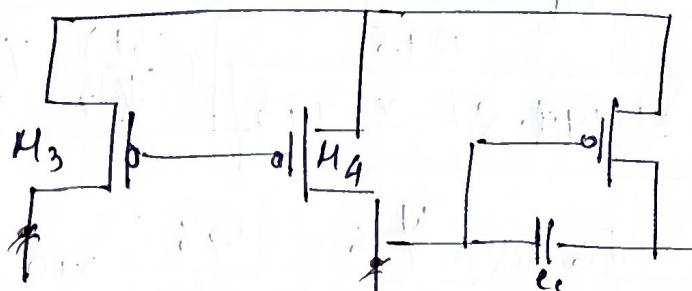

$M_3 \rightarrow M_4 \rightarrow$ Current Mirror. It means, $(V_{g_3} = V_{g_4})$; $(V_{D_3} = V_{D_4})$

$(r_{s_3} = r_{s_4})$; $\therefore V_{g_3} = V_{g_4}$ and $V_{sD_3} = V_{sD_4}$

$$\therefore V_{g_6} = V_{D_4} = V_{D_3} = V_{g_3}$$

$$\text{also, } \boxed{V_{gs_3} = V_{gs_4} = V_{gs_6}}$$

$$I_0 = \mu_p \cos(\omega_L) \left[\frac{(V_{gs} - V_t)^2}{2} \right]$$

$$\therefore \left(\frac{W}{L} \right) \propto I_0$$

$$\frac{(\omega_L)_6}{(\omega_L)_4} = \frac{I_{D6}}{I_{D4}} = \frac{g_{m6}}{g_{m4}}$$

$$g_{m4} = \sqrt{\mu_p \cos(\omega_L) 2 I_0}$$

$$= \sqrt{60 \times 14 \times 2 \times 10}$$

$$= 129.61$$

$$\therefore \left(\frac{W}{L} \right)_6 = \left(\frac{W}{L} \right)_4 \times \frac{g_{m6}}{g_{m4}}$$

$$= 14 \times \frac{1600}{129.61}$$

$$\boxed{\left(\frac{W}{L} \right)_6 \approx 192.82 \approx 193} \quad \boxed{\left(\frac{W}{L} \right)_7 = 75}$$

Design I_7

$$\frac{I_6}{I_7} = \frac{\left(\frac{W}{L} \right)_6}{\left(\frac{W}{L} \right)_7} = \frac{194}{14} \times 10$$

$$\Rightarrow \boxed{I_6 = 124.28} \quad \boxed{125}$$

$$\frac{I_7}{I_5} = \frac{\left(\frac{W}{L} \right)_7}{\left(\frac{W}{L} \right)_5} = \Rightarrow \left(\frac{W}{L} \right)_7 = \frac{I_7}{I_5} \times \left(\frac{W}{L} \right)_5$$

$$\Rightarrow \cancel{I_7} = \cancel{\frac{\left(\frac{W}{L} \right)_7}{\left(\frac{W}{L} \right)_5} \times I_5} = \frac{125}{20} \times 12 = \frac{15}{20} \times 12 \\ = 75$$

